

Jyresa Mae M. Amboang
Frances Nicole S. Gigataras
Crishelle A. Agopitac
Erica Dianne Q. Canillo
Laboratory Submitted: June 13, 2022
Laboratory Hours: 504 hours

Final Project Part I
Multicycle ARM Processor (Part I)

Main FSM output table

State (Name)	FSM Control Word											
	NextPC	Branch	MemW	RegW	IRWrite	AdrSrc	ResultSrc _{C1} :0		ALUSrcA ₁ :0		ALUSrcB ₁ :0	ALUOp
	1	0	0	0	1	0	10	0	1	10	0	0x114C
	0	0	0	0	0	0	10	0	1	10	0	0x004C
	0	0	0	0	0	0	00	0	0	01	0	0x0002
	0	0	0	0	0	1	00	0	0	00	0	0x0080
	0	0	0	1	0	0	01	0	0	00	0	0x0220
	0	0	1	0	0	1	00	0	0	00	0	0x0480
	0	0	0	0	0	0	00	0	0	00	1	0x0001
	0	0	0	0	0	0	00	0	0	01	1	0x0003
	0	0	0	1	0	0	00	0	0	00	0	0x0200
	0	1	0	0	0	0	10	1	0	01	0	0x0852

Table 1. Main FSM output

SystemVerilog Code for Datapath

```
module datapath(input logic      clk, reset,
               output logic [31:0] Addr, WriteData,
               input  logic [31:0] ReadData,
               output logic [31:0] Instr,
               output logic [3:0]  ALUFlags,
               input  logic      PCWrite, RegWrite,
               input  logic      IRWrite,
               input  logic      AddrSrc,
               input  logic [1:0] RegSrc,
               input  logic [1:0] ALUSrcA, ALUSrcB, ResultSrc,
               input  logic [1:0] ImmSrc, ALUControl);

logic [31:0] PCNext, PC;
logic [31:0] ExtImm, SrcA, SrcB, Result;
logic [31:0] Data, RD1, RD2, A, ALUResult, ALUOut;
logic [3:0]  RA1, RA2;

// next PC logic
floprn #(32) pcreg(clk, reset, PCWrite, Result, PC);

// memory logic
mux2 #(32)  adrmux(PC, ALUOut, AddrSrc, Addr);
floprn #(32) ir(clk, reset, IRWrite, ReadData, Instr);
flopr  #(32) datareg(clk, reset, ReadData, Data);

// register file logic
mux2 #(4)  ra1mux(Instr[19:16], 4'b1111, RegSrc[0], RA1);
mux2 #(4)  ra2mux(Instr[3:0], Instr[15:12], RegSrc[1], RA2);
regfile   rf(clk, RegWrite, RA1, RA2,
             Instr[15:12], Result, Result,
             RD1, RD2);
flopr #(32) srcareg(clk, reset, RD1, A);
flopr #(32) wdreg(clk, reset, RD2, WriteData);
extend   ext(Instr[23:0], ImmSrc, ExtImm);

// ALU logic
mux3 #(32) srcamux(A, PC, ALUOut, ALUSrcA, SrcA);
mux3 #(32) srcbmux(WriteData, ExtImm, 32'd4, ALUSrcB, SrcB);
alu       alu(SrcA, SrcB, ALUControl, ALUResult, ALUFlags);
```

```
flopr #(32) aluoutreg(clk, reset, ALUResult, ALUOut);
mux3 #(32) resmux(ALUOut, Data, ALUResult, ResultSrc, Result);
endmodule
```

ModelSim Simulation (clk, reset, PC, Instr, state, and ALUResult)
SystemVerilog of the Controller unit

```
module controller(input logic      clk,
                  input logic      reset,
                  input logic [31:12] Instr,
                  input logic [3:0]  ALUFlags,
                  output logic      PCWrite,
                  output logic      MemWrite,
                  output logic      RegWrite,
                  output logic      IRWrite,
                  output logic      AddrSrc,
                  output logic [1:0] RegSrc,
                  output logic [1:0] ALUSrcA,
                  output logic [1:0] ALUSrcB,
                  output logic [1:0] ResultSrc,
                  output logic [1:0] ImmSrc,
                  output logic [1:0] ALUControl);

logic [1:0] FlagW;
logic      PCS, NextPC, RegW, MemW;

decode dec(clk, reset, Instr[27:26], Instr[25:20], Instr[15:12],
           FlagW, PCS, NextPC, RegW, MemW,
           IRWrite, AddrSrc, ResultSrc,
           ALUSrcA, ALUSrcB, ImmSrc, RegSrc, ALUControl);
condlogic cl(clk, reset, Instr[31:28], ALUFlags,
             FlagW, PCS, NextPC, RegW, MemW,
             PCWrite, RegWrite, MemWrite);
endmodule
```

```
module decode(input logic      clk, reset,
              input logic [1:0] Op,
              input logic [5:0] Funct,
              input logic [3:0] Rd,
              output logic [1:0] FlagW,
              output logic      PCS, NextPC, RegW, MemW,
```

```

    output logic    IRWrite, AddrSrc,
    output logic [1:0] ResultSrc, ALUSrcA, ALUSrcB,
    output logic [1:0] ImmSrc, RegSrc, ALUControl);

logic    Branch, ALUOp;

// Main FSM
mainfsm fsm(clk, reset, Op, Funct,
            IRWrite, AddrSrc,
            ALUSrcA, ALUSrcB, ResultSrc,
            NextPC, RegW, MemW, Branch, ALUOp);

// ADD CODE BELOW
// Add code for the ALU Decoder and PC Logic.
// Remember, you may reuse code from previous labs.
// ALU Decoder
always_comb
    if (ALUOp) begin          // which Data-processing Instr?
        case(Funct[4:1])
            4'b0100: ALUControl = 2'b00; // ADD
            4'b0010: ALUControl = 2'b01; // SUB
            4'b0000: ALUControl = 2'b10; // AND
            4'b1100: ALUControl = 2'b11; // ORR
            default: ALUControl = 2'bx; // unimplemented
        endcase
        FlagW[1]    = Funct[0]; // update N & Z flags if S bit is set
        FlagW[0]    = Funct[0] & (ALUControl == 2'b00 | ALUControl == 2'b01);
    end else begin
        ALUControl = 2'b00; // add for non data-processing instructions
        FlagW      = 2'b00; // don't update Flags
    end

// PC Logic
assign PCS = ((Rd == 4'b1111) & RegW) | Branch;

// Add code for the Instruction Decoder (Instr Decoder) below.
// Recall that the input to Instr Decoder is Op, and the outputs are
// ImmSrc and RegSrc. We've completed the ImmSrc logic for you.

// Instr Decoder
assign ImmSrc    = Op;
assign RegSrc[0] = (Op == 2'b10); // read PC on Branch

```

```

    assign RegSrc[1] = (Op == 2'b01); // read Rd on STR

endmodule

module mainfsm(input logic    clk,
               input logic    reset,
               input logic [1:0] Op,
               input logic [5:0] Funct,
               output logic    IRWrite,
               output logic    AddrSrc,
               output logic [1:0] ALUSrcA, ALUSrcB, ResultSrc,
               output logic    NextPC, RegW, MemW, Branch, ALUOp);

    typedef enum logic [3:0] {FETCH, DECODE, MEMADR, MEMRD, MEMWB,
                              MEMWR, EXECUTER, EXECUTEI, ALUWB, BRANCH,
                              UNKNOWN}

    statetype;

    statetype state, nextstate;
    logic [12:0] controls;

    // state register
    always @(posedge clk or posedge reset)
        if (reset) state <= FETCH;
        else state <= nextstate;

    // ADD CODE BELOW
    // Finish entering the next state logic below. We've completed the
    // first two states, FETCH and DECODE, for you.

    // next state logic
    always_comb
        casex(state)
            FETCH:          nextstate = DECODE;
            DECODE: case(Op)
                2'b00:
                    if (Funct[5]) nextstate = EXECUTEI;
                    else          nextstate = EXECUTER;
                2'b01:      nextstate = MEMADR;
                2'b10:      nextstate = BRANCH;
                default:    nextstate = UNKNOWN;
            endcase

```

```

EXECUTER:      nextstate = ALUWB;
EXECUTEI:      nextstate = ALUWB;
MEMADR:
  if (Funct[0]) nextstate = MEMRD;
  else          nextstate = MEMWR;
MEMRD:         nextstate = MEMWB;
default:       nextstate = FETCH;
endcase

// ADD CODE BELOW
// Finish entering the output logic below. We've entered the
// output logic for the first two states, FETCH and DECODE, for you.

// state-dependent output logic
always_comb
case(state)
  FETCH:  controls = 13'b10001_010_01100;
  DECODE: controls = 13'b00000_010_01100;
  EXECUTER: controls = 13'b00000_000_00001;
  EXECUTEI: controls = 13'b00000_000_00011;
  ALUWB:   controls = 13'b00010_000_00000;
  MEMADR:  controls = 13'b00000_000_00010;
  MEMWR:   controls = 13'b00100_100_00000;
  MEMRD:   controls = 13'b00000_100_00000;
  MEMWB:   controls = 13'b00010_001_00000;
  BRANCH:  controls = 13'b01000_010_10010;
  default: controls = 13'bxxxxx_xxx_xxxxx;
endcase

assign {NextPC, Branch, MemW, RegW, IRWrite,
      AddrSrc, ResultSrc,
      ALUSrcA, ALUSrcB, ALUOp} = controls;
endmodule

// ADD CODE BELOW
// Add code for the condlogic and condcheck modules. Remember, you may
// reuse code from prior labs.
module condlogic(input logic clk, reset,
  input logic [3:0] Cond,
  input logic [3:0] ALUFlags,
  input logic [1:0] FlagW,
  input logic PCS, NextPC, RegW, MemW,

```

```

  output logic PCWrite, RegWrite, MemWrite);

logic [1:0] FlagWrite;
logic [3:0] Flags;
logic CondEx, CondExDelayed;

// ADD CODE HERE
flopnr #(2)flagreg1(clk, reset, FlagWrite[1], ALUFlags[3:2],
Flags[3:2]);
flopnr #(2)flagreg0(clk, reset, FlagWrite[0], ALUFlags[1:0],
Flags[1:0]);

// write controls are conditional
condcheck cc(Cond, Flags, CondEx);
flopnr #(1)condreg(clk, reset, CondEx, CondExDelayed);
assign FlagWrite = FlagW & {2{CondEx}};
assign RegWrite = RegW & CondExDelayed;
assign MemWrite = MemW & CondExDelayed;
assign PCWrite = (PCS & CondExDelayed) | NextPC;
endmodule

module condcheck(input logic [3:0] Cond,
  input logic [3:0] Flags,
  output logic CondEx);

// ADD CODE HERE
logic neg, zero, carry, overflow, ge;

assign {neg, zero, carry, overflow} = Flags;
assign ge = (neg == overflow);

always_comb
case(Cond)
  4'b0000: CondEx = zero; // EQ
  4'b0001: CondEx = ~zero; // NE
  4'b0010: CondEx = carry; // CS
  4'b0011: CondEx = ~carry; // CC
  4'b0100: CondEx = neg; // MI
  4'b0101: CondEx = ~neg; // PL
  4'b0110: CondEx = overflow; // VS
  4'b0111: CondEx = ~overflow; // VC
  4'b1000: CondEx = carry & ~zero; // HI

```

```

4'b1001: CondEx = ~(carry & ~zero); // LS
4'b1010: CondEx = ge;           // GE
4'b1011: CondEx = ~ge;          // LT
4'b1100: CondEx = ~zero & ge;    // GT
4'b1101: CondEx = ~(~zero & ge); // LE
4'b1110: CondEx = 1'b1;         // Always
default: CondEx = 1'bx;         // undefined
endcase
endmodule

```

Testbench

```
module testbench2();
```

```

// controller inputs
logic    clk;
logic    reset;
logic [19:0] Instr;
logic [3:0] ALUFlags;

```

```

// controller outputs
logic    PCWrite, MemWrite, RegWrite, IRWrite, AddrSrc;
logic [1:0] RegSrc, ALUSrcA, ALUSrcB, ResultSrc, ImmSrc, ALUControl;

```

```

// define Cmd fields for data-processing instructions
parameter ADD    = 4'b0100;
parameter SUB    = 4'b0010;
parameter AND    = 4'b0000;
parameter ORR    = 4'b1100;

```

```

// Sub-fields of Instr[31:12]
logic [3:0] Cond;
logic [1:0] Op;
logic [5:0] Funct;
logic [3:0] Rd;

```

```
assign Instr = {Cond, Op, Funct, 4'b0, Rd};
```

```

// instantiate dut
controller dut(clk, reset, Instr, ALUFlags,

```

```

PCWrite, MemWrite, RegWrite, IRWrite, AddrSrc,
RegSrc, ALUSrcA, ALUSrcB, ResultSrc, ImmSrc,
ALUControl);

```

```

// generate clock to sequence tests
always
begin
    clk <= 1; # 5; clk <= 0; # 5;
end

```

```

// apply inputs; user must manually verify outputs
initial
begin
    // reset controller
    reset = 1; #12; reset = 0;

```

```

// test LDR
    assign Cond = 4'b1110; assign Op = 2'b01;
    assign Funct = 6'b011001; assign Rd = 8'b1110;
    assign ALUFlags = 4'b0111;
    #50; // run 5 cycles

```

```

// test STR
    assign Cond = 4'b1110; assign Op = 2'b01;
    assign Funct = 6'b011000; assign Rd = 8'b0010;
    assign ALUFlags = 4'b1000;
    #40; // run 4 cycles

```

```

// test ADD – immediate Src2
    assign Cond = 4'b1110; assign Op = 2'b00;
    assign Funct = {1'b1, ADD, 1'b0}; assign Rd = 8'b0100;
    assign ALUFlags = 4'b0110;
    # 40; // run 4 cycles

```

```

// test ADD – register Src2, set condition flags, Rd = PC
    assign Cond = 4'b1110; assign Op = 2'b00;
    assign Funct = {1'b0, ADD, 1'b1}; assign Rd = 8'b1111;
    assign ALUFlags = 4'b1000;
    # 40; // run 4 cycles

```

```

// test SUB – immediate Src2, conditional execution (LE),
// set condition flags

```

```
// should be executed
assign Cond = 4'b1101; assign Op = 2'b00;
assign Funct = {1'b1, SUB, 1'b1}; assign Rd = 8'b0111;
assign ALUFlags = 4'b1001;
# 40;    // run 4 cycles
```

```
// test AND – register Src2, Rd = PC, cond. execution (LT)
// shouldn't be executed
assign Cond = 4'b1011; assign Op = 2'b00;
assign Funct = {1'b0, AND, 1'b0}; assign Rd = 8'b1111;
assign ALUFlags = 4'b1110;
# 40;    // run 4 cycles
```


```
// test ORR – immediate Src2, set Flags[3:2] (i.e., N,Z)
assign Cond = 4'b1110; assign Op = 2'b00;
assign Funct = {1'b1, ORR, 1'b1}; assign Rd = 8'b0110;
assign ALUFlags = 4'b1000;
# 40;    // run 4 cycles
```


```
// test B (taken)
assign Cond = 4'b1110; assign Op = 2'b10;
assign Funct = 6'b100000; assign Rd = 8'b0;
assign ALUFlags = 4'b1011;
# 30;    // run 3 cycles
```

```
// test B (not taken) EQ condition mnemonic
assign Cond = 4'b0000; assign Op = 2'b10;
assign Funct = 6'b101110; assign Rd = 8'b1111;
assign ALUFlags = 4'b1101;
# 30;    // run 3 cycles
```

```
end
endmodule
```

 ModelSim Waveforms: CLK, Reset, Cond, OP, Funct, Rd, ALUFlags, ALUControl, ImmSrc, RegSrc, RegWrite,MemWrite, PCWrite, state, and the entire control word (i.e. the 4-nibble word you entered in Table 1).



 

CONCLUSION:

What did we learn or take away from performing this Final Project Part I?

This lab exercise will teach us essential information about digital hardware design. To explore the implication of processor design and function, we will construct a simplified ARM single-cycle processor in SystemVerilog, and the ALU and register file, among other submodules of the control and datapath units, will become more apparent to us. SystemVerilog coding improves our expertise with hardware description languages, letting us describe complicated hardware designs in a condensed form. In this lab, we will enhance encoding strategies to strengthen the implementation of the CPU, with a focus on increasing hardware design efficiency. We'll also build testbeds and write test scripts to ensure our designs are sound. By utilizing ModelSim to simulate the CPU, our understanding of digital circuit analysis and interpretation has been dramatically improved. In addition to learning about ARM architecture and processor design, we can improve our problem-solving, debugging, and communication skills in this laboratory activity. These abilities will be essential for any digital hardware engineering initiatives we may do in the future.